

# GITIANKOLA

## ITI Quiz - 06-Mar-2026 01:45 PM

Q. ID: ITISKILL4196QY | March 2026

64.00% 16 / 25

Student Name	Shreekar gouda	Access Code	5868
Attempt No.	#1	Completion Time	02:14 PM
Rank	#12	Total Questions	25

16 SCORE

25 MAX MARKS

16 CORRECT

9 INCORRECT

### Answer Review

Q1 **CORRECT** How many transistors are built inside the Very Large Scale Integration (VLSI) IC package?

A. 1000 and above

B. 1 to 10 transistors

C. 10 to 100 transistors

D. 100 to 1000 transistors

Q2 **INCORRECT** Which IC package consist of 100 to 1000 transistors?

A. Large scale integration (LSI)

B. Small scale integration (SSI)

C. Medium scale integration (MSI)

D. Very large scale integration (VLSI)

Q3 **CORRECT** Which is the 3 terminal, negative voltage regulator IC?

A. LM 320

B. LM 340

C. IC 7905

D. IC 7812

Q4 **CORRECT** Which three terminal voltage regulator IC has adjustable output?

A. LM 100

B. LM 105

C. LM 305

D. LM 317

Q5 **INCORRECT** How much is the maximum load current of the negative voltage regulator IC 7912?

A. 1.0 A

B. 1.5 A

C. 2.0 A

D. 0.55 A

Q6 **CORRECT** What is the current rating of voltage regulator IC LM338K?

A. 2A

B. 3A

C. 4A

D. 5A

Q7 **CORRECT** Which method is followed to troubleshoot the problem causing section by the symptom?

A. Step by step method

B. Sensory test method

C. Trial and error method

D. Logical approach method

Q8 **INCORRECT** Which type of voltage regulator is IC 723?

A. Multipin variable voltage regulator

B. Three pin positive voltage regulator

C. Three pin negative voltage regulator

D. Three pin adjustable voltage regulator

Q9 **CORRECT** Which component filter the ripples in the rectifier circuit?

A. DIAC

B. Diode

C. TRIAC

D. Capacitor

Q10 **CORRECT** Which parameter is maintained constant in zener diode?

A. Power

B. Current

C. Voltage

D. Resistance

Q11 **INCORRECT** What is the meaning of maximum safe reverse voltage across a diode?

- A. PIV voltage
- B. Knee voltage
- C. Break down voltage
- D. Reverse break down voltage

Q12 **CORRECT** When does the zener diode begins to conduct in the reverse biased condition?

- A. When bias voltage reached 0.7V
- B. After the barrier voltage cancelled
- C. Voltage across zener reached 0.3V
- D. Voltage across it reached the zener voltage

Q13 **CORRECT** What is the output pulse frequency of the full wave rectifier with input frequency of 50 Hz?

- A. 40 Hz
- B. 60 Hz
- C. 100 Hz
- D. 200 Hz

Q14 **CORRECT** What is the maximum safe reverse voltage rating of a diode?

- A. PIV voltage
- B. Knee voltage
- C. Break down voltage
- D. Forward break down voltage

Q15 **INCORRECT** Which is the first step followed in troubleshooting of electronic circuit?

A. Thermal test

B. Chemical test

C. Mechanical test

D. Physical and sensory test

Q16 **INCORRECT** Which diode is used in low power communication circuits?

A. Signal diodes

B. Rectifier diodes

C. Switching diodes

D. High power diodes

Q17 **CORRECT** What is the disadvantage of the two diode full wave rectifier compared with a bridge rectifier?

A. DC output level is higher

B. The ripple frequency is higher

C. The need of bulky transformer

D. Each diode carries half the load current

Q18 **CORRECT** What is the process of adding impurities to a pure semi conductor material?

A. Doping

B. Etching

C. Forming

D. Diffusion

Q19 **CORRECT** Which impurity is added to form P - type semiconductor material?

A. Arsenic

B. Gallium

C. Antimony

D. Phosphorus

Q20 **CORRECT** Which impurity is added to pure semiconductor to form N-type material?

A. Boron

B. Indium

C. Arsenic

D. Gallium

Q21 **INCORRECT** What is the output frequency of the pulsating DC in a two diode fullwave rectifier?

A. Half of the input A/C frequency

B. Double the input A/C frequency

C. Same frequency of the A/C input

D. Three times the input A/C frequency

Q22 **INCORRECT** What is the name of the process of converting AC into DC voltage?

A. Inverting

B. Rectifying

C. Amplifying

D. Demodulating

**Q23** **CORRECT** What is the effect on the output voltage in a bridge rectifier circuits, with one diode open?

- A. Very low voltage
- B. No output DC voltage
- C. Full output rated voltage
- D. Half of the rated output voltage

**Q24** **CORRECT** What is the peak to peak voltage in a bridge rectifier circuit with load current of 10 mA, capacitance of 470 F and 50 Hz supply frequency?

- A. 0.213 v
- B. 1.525 v
- C. 2.134 v
- D. 3.567 v

**Q25** **INCORRECT** What is the minimum current rating of four diode bridge rectifier to supply load current of 1.8 Amp?

- A. 0.9 Amp
- B. 1.8 Amp
- C. 2.0 Amp
- D. 5.0 Amp