

Duration: 30 Mins

Total Marks: 25

Q.ID: ITISKILL3379EU

1. What is the total resistance if two resistances of 4 ohms and 6 ohms are connected in parallel?

- A) 5
B) 4
C) 2.4
D) 10

Answer: C) 2.4

2. Which law states about electromagnetic induction?

- A) Ohm's law
B) Lenz's law
C) Hooke's law
D) Faraday's law

Answer: D) Faraday's law

3. What is the power if an emf of one volt causes a current flow of 1ampere?

- A) 1 HP
B) 1 kilowatt
C) 1 watt
D) 1 Kilowatt hour

Answer: C) 1 watt

4. How many hours will take for a 100 watts bulb to consume 1 kwh energy? $W = 1 \text{ Kwh}$ $P = 100 \text{ Watts}$ $t = \text{_____Hours}$

- A) 12 hours
B) 24 hours
C) 10 hours
D) 18 hours

Answer: C) 10 hours

5. Which statement is correct according to ohm's law?

- A) $I = R/V$
B) $I = V/R$
C) $I = 1/V$
D) $I = R$

Answer: B) $I = V/R$

6. What is the current? $R = 50 \text{ Ohms}$ 220 Volts $I = \text{_____Amps}$

- A) 4.1 Amps
B) 4.4 Amps
C) 4.2 Amps
D) 4.3 Amps

Answer: B) 4.4 Amps

7. Which is the example for statically induced emf?

- A) Refrigerator
B) Motor
C) Transformer
D) Generator

Answer: C) Transformer

8. How much voltage will be required to illuminate a 40 watts fluorescent lamp draws a current of 0.10 amperes?

- A) 390 volts
B) 405 volts

- C) 395 volts
D) 400 volts

Answer: D) 400 volts

9. What is the voltage? $R = 250 \text{ Ohms}$ $I = 0.44 \text{ Amps}$ $V = \text{_____Volts}$

- A) 108 Volts
B) 110 Volts
C) 105 Volts
D) 100 Volts

Answer: B) 110 Volts

10. Which law states that at constant temperature the current passing through a closed circuit is directly proportional to the potential difference and inversely proportional to the resistance?

- A) Lenz's law
B) Hooke's law
C) Newton's law
D) Ohm's law

Answer: D) Ohm's law

11. Which is equal to electric power?

- A) $I^2 R$ watts
B) IR
C) $R^2 I$ watts
D) RI

Answer: A) $I^2 R$ watts

12. Which is the unit of current?

- A) Ampere
B) Volt
C) Ohm
D) Watt

Answer: A) Ampere

13. Which is mineral insulator

- A) Porcelain
B) Glass
C) Mica
D) Quartz

Answer: C) Mica

14. What does EMF stands for?

- A) Electronic Magnetic Force
B) Electro Motive Force
C) Electromated Force
D) Electro Magnetic Force

Answer: B) Electro Motive Force

15. What is the filament resistance if a 6 volt bulb draws a current of 0.5 Amps?

- A) 10 W
B) 1.2 W
C) 12 W
D) 3 W

Answer: C) 12 W

16. What is the current Flow in the bulb? $P = 550 \text{ watts}$

$R = 22 \text{ Ohms}$ $I = \underline{\hspace{1cm}}$ Amps

- A) 4 Amps
- B) 2 Amps
- C) 3 Amps
- D) 5 Amps

Answer: D) 5 Amps

17. What is the flow of electrons in any conductor?

- A) Current
- B) Resistance
- C) Power
- D) Voltage

Answer: A) Current

18. What is the formula for induced emf?

- A) $B^2 L \sin \theta$ volts
- B) $BL \sin \theta$ volts
- C) $BLV \sin \theta$ volts
- D) $B^2 V \sin \theta$ volts

Answer: C) $BLV \sin \theta$ volts

19. Which is the example for dynamically induced Emf?

- A) Generator
- B) Car
- C) Motor
- D) Motor bike

Answer: A) Generator

20. What is the resistance of an electric iron if the rating of electric iron is 220 V and 500 watts?

- A) 94.8 ohms
- B) 96.8 ohms
- C) 97.8 ohms
- D) 95.8 ohms

Answer: B) 96.8 ohms

21. What is the total resistance if three resistances of 3 ohms, 9 ohms and 5 ohms are connected in series?

- A) 1/17 ohms
- B) 7 ohm
- C) 17 ohms
- D) 11 ohms

Answer: C) 17 ohms

22. Which is the unit electrical power?

- A) Ampere
- B) Watts
- C) Ohms
- D) Volts

Answer: B) Watts

23. What is the rated power if an adjustable resistor bears the following label 1.5 k ohms/ 0.08A?

- A) 9.2 watts
- B) 9.8 watts
- C) 9.4 watts
- D) 9.6 watts

Answer: D) 9.6 watts

24. What is the unit of intensity of magnetic field?

- A) Coloumb
- B) Hertz
- C) wb/m
- D) m/wb

Answer: C) wb/m

25. What is the power required? $I = 0.455 \text{ Amps}$ $R = 484 \text{ Ohms}$ $P = \underline{\hspace{1cm}}$ Watts

- A) 99.2 watts
- B) 98.2 watts
- C) 101.2 watts
- D) 100.2 watts

Answer: D) 100.2 watts
