

Duration: 30 Mins

Total Marks: 25

ID: ITISKILL3379EU

Student Name: _____ Roll No: _____

1. Which is the example for statically induced emf?

- A) Generator B) Refrigerator
C) Motor D) Transformer

- A) Electromated Force B) Electronic Magnetic Force
C) Electro Magnetic Force D) Electro Motive Force

**2. What is the current Flow in the bulb?
 P = 550 watts

 R = 22 Ohms
 I = _____Amps**

- A) 5 Amps B) 4 Amps
C) 3 Amps D) 2 Amps

10. What is the flow of electrons in any conductor?

- A) Power B) Voltage
C) Current D) Resistance

3. What is the unit of intensity of magnetic field?

- A) Hertz B) Coloumb
C) wb/m D) m/wb

11. What is the total resistance if two resistances of 4 ohms and 6 ohms are connected in parallel?

- A) 4 B) 10
C) 2.4 D) 5

4. Which law states that at constant temperature the current passing through a closed circuit is directly proportional to the potential difference and inversely proportional to the resistance?

- A) Hooke's law B) Lenz's law
C) Ohm's law D) Newton's law

12. What is the filament resistance if a 6 volt bulb draws a current of 0.5 Amps?

- A) 10 W B) 12 W
C) 1.2 W D) 3 W

5. Which is the unit of current?

- A) Ampere B) Volt
C) Ohm D) Watt

**13. What is the power required?
 I = 0.455 Amps
 R = 484 Ohms
 P = _____Watts**

- A) 101.2 watts B) 98.2 watts
C) 99.2 watts D) 100.2 watts

6. What is the power if an emf of one volt causes a current flow of 1ampere?

- A) 1 HP B) 1 watt
C) 1 kilowatt D) 1 Kilowatt hour

14. Which is mineral insulator

- A) Glass B) Porcelain
C) Quartz D) Mica

7. What is the total resistance if three resistances of 3 ohms, 9 ohms and 5 ohms are connected in series?

- A) 1/17 ohms B) 7 ohm
C) 17 ohms D) 11 ohms

15. Which statement is correct according to ohm's law?

- A) $I = R/V$ B) $I = 1/V$
C) $I = V/R$ D) $I = R$

8. What is the rated power if an adjustable resistor bears the following label 1.5 k ohms/ 0.08A?

- A) 9.4 watts B) 9.2 watts
C) 9.8 watts D) 9.6 watts

16. Which law states about electromagnetic induction?

- A) Lenz's law B) Faraday's law
C) Ohm's law D) Hooke's law

9. What does EMF stands for?

**17. How many hours will take for a 100 watts bulb to consume 1 kwh energy?
 W = 1 Kwh
 P = 100 Watts
 t = _____Hours**

- A) 24 hours B) 18 hours
C) 12 hours D) 10 hours

18. Which is equal to electric power?

- A) IR
- B) $R^2 I$ watts
- C) RI
- D) $I^2 R$ watts

19. What is the voltage? $R = 250$ Ohms $I = 0.44$ Amps $V =$ ____ Volts

- A) 100 Volts
- B) 110 Volts
- C) 105 Volts
- D) 108 Volts

20. How much voltage will be required to illuminate a 40 watts fluorescent lamp draws a current of 0.10 amperes?

- A) 400 volts
- B) 390 volts
- C) 395 volts
- D) 405 volts

21. What is the resistance of an electric iron if the rating of electric iron is 220 V and 500 watts?

- A) 95.8 ohms
- B) 96.8 ohms
- C) 94.8 ohms
- D) 97.8 ohms

22. Which is the example for dynamically induced Emf?

- A) Generator
- B) Car
- C) Motor bike
- D) Motor

23. What is the formula for induced emf?

- A) $B^2 V \sin \theta$ volts
- B) $BL \sin \theta$ volts
- C) $B^2 L \sin \theta$ volts
- D) $BLV \sin \theta$ volts

24. Which is the unit electrical power?

- A) Ohms
- B) Volts
- C) Ampere
- D) Watts

25. What is the current? $R = 50$ Ohms $V = 220$ Volts $I =$ ____ Amps

- A) 4.3 Amps
- B) 4.1 Amps
- C) 4.4 Amps
- D) 4.2 Amps