

Monthly test

Q. ID: ITISKILL68278M

February 2026

Govt ITI Beguru

Answer Key

Duration: 30 Mins

Total Marks: 32

Q.ID: ITISKILL68278M

1. What is the efficiency transformer coupled class A amplifier?

- A) More than 60%
- B) About 50%
- C) Unity
- D) Less than 20%

Answer: B) About 50%

2. What will happen when the forward bias voltage across the PN junction is increased excessively?

- A) Barrier width of junction increases
- B) Increases the cut-in voltage
- C) Junction ruptured and short circuited
- D) No current flows through the junction

Answer: C) Junction ruptured and short circuited

3. What is the current gain of a common emitter amplifier?

- A) Less than 1
- B) Infinity
- C) Greater than 1
- D) Unity

Answer: A) Less than 1

4. Which type of amplifier is used to operate the loud speaker?

- A) Power amplifier
- B) IF amplifier
- C) RF amplifier
- D) Voltage amplifier

Answer: A) Power amplifier

5. What is the advantage of using bias in transistor circuits?

- A) Provides positive feedback
- B) Easily sets saturation
- C) Never reach saturation
- D) Gives maximum distortion

Answer: C) Never reach saturation

6. How do the values of bias resistors selected for collector current in class-B amplifiers?

- A) Quiescent current at mid point
- B) Quiescent current beyond the cut-off point
- C) Q point set slightly below cut-off
- D) Quiescent current over the cut-off value

Answer: D) Quiescent current over the cut-off value

7. How is the maximum permissible voltage that can be applied across the collector-emitter junction of a transistor indicated?

- A) VCE (max) in volts
- B) VCB (max) in volts
- C) VBE (max) in volts
- D) VCC in volts

Answer: A) VCE (max) in volts

8. What is the purpose of using positive feedback in amplifiers?

- A) To produce modulation
- B) To produce oscillation
- C) To produce demodulation
- D) To produce multiplexion

Answer: B) To produce oscillation

9. Which type of amplifier is used to operate the loud speaker?

- A) IF Amplifier
- B) Power Amplifier
- C) RF Amplifier
- D) Voltage Amplifier

Answer: B) Power Amplifier

10. What type of packaging is generally used for transistors utilized for low power amplification?

- A) Plastic packaging
- B) Plastic packaging with metal heatsinks
- C) Metal packaging
- D) Ceramic packaging

Answer: A) Plastic packaging

11. Which type of transistors are required to amplify signals from the microphone/transducer?

- A) High power transistors
- B) Low power transistors
- C) Medium power transistors
- D) Epitaxial power transistors

Answer: B) Low power transistors

12. Which coding system for transistor type numbering system is followed by American standard?

- A) JIS standard
- B) Home codes
- C) PRO-ELECTRON standard
- D) JEDEC standard

Answer: D) JEDEC standard

13. Which configuration of transistor amplifier is most commonly used in electronic circuits?

- A) Common emitter configuration
- B) Common base configuration
- C) Common collector configuration
- D) Common drain amplifier configuration

Answer: A) Common emitter configuration

14. In which quantity does the Q point of a transistor amplifier?

- A) Proper biasing methods
- B) Mismatching signals
- C) Increased temperature
- D) Decreased temperature

Answer: C) Increased temperature

15. How the negative feedback is called?

- A) Regenerative feedback B) Voltage controlled feedback
C) Degenerative feedback D) Current controlled feedback

Answer: C) Degenerative feedback

16. What is the voltage gain in a transistor if the input voltage in 40mv and the output voltage in 3.6V?

- A) 45 B) 270
C) 180 D) 90

Answer: D) 90

17. Why the complementary - symmetry amplifier is preferred over the other types of amplifier configurations?

- A) To minimize the gain B) To get less distortion
C) To eliminate the transformer D) To get more voltage gain

Answer: C) To eliminate the transformer

18. What is the maximum emitter to base voltage VEB (max) for the transistor BC 147?

- A) 4V B) 8V
C) 6V D) 5V

Answer: C) 6V

19. Why NPN type of transistors are preferred over the PNP type transistors?

- A) NPN has good bias stability B) Low operating voltage
C) NPN has lower switching speed D) NPN has higher switching speed

Answer: D) NPN has higher switching speed

20. Where does the depletion region exists in a bipolar transistor?

- A) Between emitter - base electrodes B) Between collector and emitter electrodes
C) Between collector - base electrodes D) Between E-B and B-C electrodes

Answer: D) Between E-B and B-C electrodes

21. What is the overall base emitter voltage required to turn the darlington pair?

- A) 0.2 V B) 0.7 V
C) 1.4 V D) 0.3 V

Answer: C) 1.4 V

22. Which type of packaging is used to transistors utilized for medium power amplification?

- A) Plastic packaging with metal heatsinks B) Plastic packaging
C) Ceramic packaging D) Metal packaging

Answer: A) Plastic packaging with metal heatsinks

23. Why transistors made of silicon is preferred over the germanium semiconductor material?

- A) Requires complicated bias arrangement B) Silicon transistor needs low cut-in-voltage
C) Higher thermal stability D) Complex design

Answer: C) Higher thermal stability

24. What is the advantage of silicon over germanium for transistor fabrication?

- A) Higher amplification factor B) Lower thermal stability
C) Lower operating voltage D) Higher thermal stability

Answer: D) Higher thermal stability

25. How can you confirm a transistor as defective?

- A) By voltage measurements B) By ohm meter testing
C) By physical testing D) By circuit testing

Answer: B) By ohm meter testing

26. What is the meaning of first letter indicated in the transistor code number BC 107?

- A) Indium material used B) Antimony material used
C) Germanium material used D) Silicon material used

Answer: D) Silicon material used

27. What is the current gain of common collector amplifier?

- A) High B) Low
C) Very high D) Medium

Answer: C) Very high

28. What is the formula used to calculate the current gain (alpha) of common base amplifier?

- A) I_E / I_C B) I_E / I_C
C) I_B / I_E D) I_C / I_E

Answer: D) I_C / I_E

29. Which parameter of passive component can be calculated using the formula ?

- A) Capacitive reactance B) Capacitance
C) Inductive reactance D) Inductance

Answer: A) Capacitive reactance

30. Which class of amplifier uses fixed bias because of its inherent advantage of transistor will never go to saturation?

- A) Class - C B) Class - AB
C) Class - A D) Class - B

Answer: C) Class - A

31. What is the input impedance of darlington pair transistors?

- A) Medium input impedance B) Very high input impedance
C) Uniter D) Very low input impedance

Answer: B) Very high input impedance

32. What is the name of multi-stage amplifiers?

- A) Cascoded amplifier B) Complementry symmetry amplifier
C) Darlington pair amplifier D) Cascaded amplifier

Answer: D) Cascaded amplifier
