

ITI Quiz - 24-Mar-2026 11:11 AM

Q. ID: ITISKILL8178HX

Oscillator module QP
14MCQ

March 2026

Sri Mahalingeswara ITI

Question Paper

Student: Amith gowda hn

Score: 5/14 (35.71%)

Code: 2616

1. What is the natural shape of a quartz crystal?

- A) Cylindrical shape with pyramid at ends (Incorrect) B) Cube shape with pyramid at ends
C) Pentagonal prism with pyramid at ends **D) Hexagonal prism with pyramid at ends**

2. What is the resonant frequency range of a crystal?

- A) Between 0.1 and 1MHZ B) Between 0.1 and 10 MHZ
C) Between 0.5 and 25 MHZ (Incorrect) **D) Between 0.5 and 30 Mhz**

3. What is the difference of Colpitts oscillator compare to Hartley oscillator?

- A) Uses split inductor B) **Uses split capacitor**
C) Uses crystal oscillator D) Uses SCR combination (Incorrect)

4. Which circuit is determined by the frequency of LC tank circuit?

- A) Oscillator** B) Amplifier (Incorrect)
C) Multiplexed D) Demodulator

5. What is the percentage of charge accumulated by the capacitor at the end of 2 time constant limit?

- A) 0.4 (Incorrect) B) 0.5
C) 0.632 **D) 0.864**

6. How many time constants required to change a capacitor to 63.2% of its full charge voltage?

- A) Four time constant B) Three time constant (Incorrect)
C) Two time constant **D) One time constant**

7. Which circuits commonly use parallel-fed Hartley oscillators?

- A) Stereo amplifiers B) **Radio receivers (Correct)**
C) Television receivers D) Automatic voltage stabilizers

8. What type of arrangement is required to sustain the oscillations of the oscillator circuit?

- A) Provide negative feedback (Incorrect) **B) Provide regenerative feedback**
C) Increase the bias voltage D) Increase the value of inductor

9. What type of feed back is used by the Wein-bridge oscillator to oscillate the signal?

- A) No feedback B) Positive feedback
C) Negative feedback **D) Both positive and negative feedback (Correct)**

10. How to improve the frequency stability in oscillator circuits?

- A) Increase the supply voltage B) **By using quartz crystal**
C) Using L and C (Incorrect) D) Improve the property of circuits

11. Which is the transistor used to operate the Colpitts oscillator?

- A) AC 127 B) **BF 194B**
C) BC 148B D) AC 188 (Incorrect)

12. How many time constant period is required to fully charge a capacitor?

- A) 10 time constants B) 7 time constants
C) **5 time constants (Correct)** D) 3 time constants

13. How to overcome the problem of frequency drift in LC oscillators?

- A) Apply opposite polarity of signal B) Provide negative feedback
C) **Using high Q coils and good quality capacitors (Correct)** D) Increase the supply voltage

14. Why LC tuned circuits are not used in audio frequency oscillators?

- A) **LC values required is too large (Correct)** B) LC components are not available
C) LC tank circuit does not produce AF signals D) LC tank circuit operation requires high voltage