

# ITI Quiz - 24-Mar-2026 11:11 AM

Q. ID: ITISKILL8178HX

Oscillator module QP  
14MCQ

March 2026

Sri Mahalingeswara ITI

Question Paper

Student: Ramacharan

Score: 9/14 (64.29%)

Code: 9329

1. What is the natural shape of a quartz crystal?
- A) Cylindrical shape with pyramid at ends  
B) Cube shape with pyramid at ends  
C) Pentagonal prism with pyramid at ends  
D) **Hexagonal prism with pyramid at ends (Correct)**
2. What is the resonant frequency range of a crystal?
- A) Between 0.1 and 1MHz  
B) Between 0.1 and 10 MHz  
C) Between 0.5 and 25 MHz  
D) **Between 0.5 and 30 Mhz (Correct)**
3. What is the difference of Colpitts oscillator compare to Hartley oscillator?
- A) Uses split inductor  
B) **Uses split capacitor (Correct)**  
C) Uses crystal oscillator  
D) Uses SCR combination
4. Which circuit is determined by the frequency of LC tank circuit?
- A) **Oscillator (Correct)**  
B) Amplifier  
C) Multiplexed  
D) Demodulator
5. What is the percentage of charge accumulated by the capacitor at the end of 2 time constant limit?
- A) 0.4  
B) 0.5  
C) 0.632  
D) **0.864 (Correct)**
6. How many time constants required to change a capacitor to 63.2% of its full charge voltage?
- A) Four time constant  
B) Three time constant  
C) Two time constant  
D) **One time constant (Correct)**
7. Which circuits commonly use parallel-fed Hartley oscillators?
- A) Stereo amplifiers  
B) **Radio receivers (Correct)**  
C) Television receivers  
D) Automatic voltage stabilizers
8. What type of arrangement is required to sustain the oscillations of the oscillator circuit?
- A) Provide negative feedback (Incorrect)  
B) **Provide regenerative feedback**  
C) Increase the bias voltage  
D) Increase the value of inductor
9. What type of feed back is used by the Wein-bridge oscillator to oscillate the signal?
- A) No feedback  
B) Positive feedback  
C) Negative feedback  
D) **Both positive and negative feedback (Correct)**
10. How to improve the frequency stability in oscillator circuits?
- A) Increase the supply voltage (Incorrect)  
B) **By using quartz crystal**  
C) Using L and C  
D) Improve the property of circuits
11. Which is the transistor used to operate the Colpitts oscillator?
- A) AC 127  
B) **BF 194B**  
C) BC 148B (Incorrect)  
D) AC 188
12. How many time constant period is required to fully charge a capacitor?
- A) 10 time constants  
B) 7 time constants  
C) **5 time constants**  
D) 3 time constants (Incorrect)
13. How to overcome the problem of frequency drift in LC oscillators?
- A) Apply opposite polarity of signal  
B) Provide negative feedback  
C) **Using high Q coils and good quality capacitors (Correct)**  
D) Increase the supply voltage
14. Why LC tuned circuits are not used in audio frequency oscillators?
- A) **LC values required is too large**  
B) LC components are not available  
C) LC tank circuit does not produce AF signals  
D) LC tank circuit operation requires high voltage (Incorrect)