

Student: Rohit pradeep naik

Score: 21/24 (87.50%)

Code: 2060

1. How many inputs are available in the 7447 BCD-to-seven segment decoder used to drive the LED display?

- A) One
B) **Four (Correct)**
C) Seven
D) Eight

2. What is the power supply required to operate the most standard TTL ICs properly?

- A) + 1.5v to +2.5V
B) - 1.5v to - 2.5V
C) **+ 4.75v to + 5.25V (Correct)**
D) + 7.5v to + 12V

3. What is the propagation delay of the standard TTL chip?

- A) 5 ns
B) 8 ns
C) **10 ns (Correct)**
D) 12 ns

4. What is the power dissipation of the standard TTL chip?

- A) 5 mW/gate
B) **10 mW/gate (Correct)**
C) 15 mW/gate
D) 20 mW/gate

5. What is the decimal conversion number for the octal number (2374)₈?

- A) (1266)₁₀
B) **(1276)₁₀ (Correct)**
C) (1286)₁₀
D) (1296)₁₀

6. What is the digital signal value for the analog signal value 6V?

- A) 100
B) 101
C) **110 (Correct)**
D) 111

7. What is the decimal number for the binary number 0101?

- A) 4
B) **5 (Correct)**
C) 6
D) 7

8. Which IC is used for (DEMUX) function in data transmission?

- A) IC 7483
B) IC 7486
C) **74 LS 138 (Correct)**
D) 74 LS 151

9. Which circuits requires the flip - flops for their operation?

- A) Amplifier circuits
B) Oscillator circuits
C) Modulator circuits
D) **Memory circuits (Correct)**

10. What is the use of flip - flop?

- A) It stores energy
B) It stores voltage
C) It stores current
D) **It stores binary information (Correct)**

11. What is the maximum possible number of flip-flops in a decade counter?

- A) 1ⁿ
B) **2ⁿ (Correct)**
C) 2ⁿ⁺¹
D) 3ⁿ

12. What is the purpose of using IC74LS190?

- A) Attenuator
B) Comparator
C) **Up/down counter (Correct)**
D) Modulator

13. Which IC is used for the function of 4 bit shift register?

- A) IC 7404
B) IC 7447
C) IC 7493
D) **IC 7495 (Correct)**

14. What is the information stored in digital registers?

- A) Analog values
B) **Binary values (Correct)**
C) Decimal values
D) Alphanumeric values

15. How many transistors are built inside the Very Large Scale Integration (VLSI) IC package?

- A) **1000 and above (Correct)**
B) 1 to 10 transistors
C) 10 to 100 transistors
D) 100 to 1000 transistors

16. Which IC package consist of 100 to 1000 transistors?

- A) **Large scale integration (LSI)**
B) Small scale integration (SSI)
C) Medium scale integration (MSI) (Incorrect)
D) Very large scale integration (VLSI)

17. Which is the 3 terminal, negative voltage regulator IC?

- A) LM 320
B) LM 340
C) **IC 7905 (Correct)**
D) IC 7812

18. Which three terminal voltage regulator IC has adjustable output?

- A) LM 100
B) LM 105
C) LM 305
D) **LM 317 (Correct)**

19. How much is the maximum load current of the negative voltage regulator IC 7912?

- A) 1.0 A B) 1.5 A (Incorrect)
C) 2.0 A D) 0.55 A
-

20. What is the current rating of voltage regulator IC LM338K?

- A) 2A B) 3A
C) 4A **D) 5A (Correct)**
-

21. Which method is followed to troubleshoot the problem causing section by the symptom?

- A) Step by step method B) Sensory test method
C) Trial and error method **D) Logical approach method (Correct)**
-

22. What is the current rating of voltage regulator IC LM317L?

- A) 0.1 A (Correct)** B) 0.2 A
C) 0.3 A D) 0.4 A
-

23. What is the range of output voltage of regulator IC LM 317?

- A) 0 to 25 V B) 0 to 30 V
C) 0 to 32 V **D) 1.2 V to 32 V (Correct)**
-

24. Which type of voltage regulator is IC 723?

- A) Multipin variable voltage regulator (Incorrect) B) Three pin positive voltage regulator
C) Three pin negative voltage regulator **D) Three pin adjustable voltage regulator**
-