

March 2026

Sri Mahalingeswara ITI

Answer Key

**Duration: 30 Mins****Total Marks: 14****Q.ID: ITISKILL874950**

1. What is the resonant frequency range of a crystal?

- A) Between 0.5 and 30 MHz    B) Between 0.5 and 25 MHz  
C) Between 0.1 and 10 MHz    D) Between 0.1 and 1MHz

**Answer: A) Between 0.5 and 30 MHz**

2. Which circuits commonly use parallel-fed Hartley oscillators?

- A) Television receivers            B) Radio receivers  
C) Stereo amplifiers                D) Automatic voltage stabilizers

**Answer: B) Radio receivers**

3. What is the percentage of charge accumulated by the capacitor at the end of 2 time constant limit?

- A) 0.5                                    B) 0.4  
C) 0.864                                D) 0.632

**Answer: C) 0.864**

4. How many time constants required to change a capacitor to 63.2% of its full charge voltage?

- A) Four time constant                B) Two time constant  
C) Three time constant                D) One time constant

**Answer: D) One time constant**

5. What is the difference of Colpitts oscillator compare to Hartley oscillator?

- A) Uses crystal oscillator            B) Uses split inductor  
C) Uses split capacitor                D) Uses SCR combination

**Answer: C) Uses split capacitor**

6. Which is the transistor used to operate the Colpitts oscillator?

- A) AC 188                                B) BF 194B  
C) AC 127                                D) BC 148B

**Answer: B) BF 194B**

7. How to overcome the problem of frequency drift in LC oscillators?

- A) Using high Q coils and good quality capacitors    B) Increase the supply voltage  
C) Provide negative feedback    D) Apply opposite polarity of signal

**Answer: A) Using high Q coils and good quality capacitors**

8. Why LC tuned circuits are not used in audio frequency oscillators?

- A) LC components are not available            B) LC tank circuit operation requires high voltage  
C) LC tank circuit does not produce AF signals    D) LC values required is too large

**Answer: D) LC values required is too large**

9. What type of arrangement is required to sustain the oscillations of the oscillator circuit?

- A) Increase the value of inductor                    B) Increase the bias voltage  
C) Provide regenerative feedback                    D) Provide negative feedback

**Answer: C) Provide regenerative feedback**

10. How to improve the frequency stability in oscillator circuits?

- A) By using quartz crystal                    B) Increase the supply voltage  
C) Improve the property of circuits                    D) Using L and C

**Answer: A) By using quartz crystal**

11. What type of feed back is used by the Wein-bridge oscillator to oscillate the signal?

- A) Negative feedback                    B) Both positive and negative feedback  
C) No feedback                            D) Positive feedback

**Answer: B) Both positive and negative feedback**

12. What is the natural shape of a quartz crystal?

- A) Hexagonal prism with pyramid at ends            B) Pentagonal prism with pyramid at ends  
C) Cylindrical shape with pyramid at ends            D) Cube shape with pyramid at ends

**Answer: A) Hexagonal prism with pyramid at ends**

13. How many time constant period is required to fully charge a capacitor?

- A) 10 time constants                    B) 7 time constants  
C) 3 time constants                    D) 5 time constants

**Answer: D) 5 time constants**

14. Which circuit is determined by the frequency of LC tank circuit?

- A) Multiplexed
- C) Demodulator

- B) Amplifier
- D) Oscillator

**Answer: D) Oscillator**

---