

# Monthly Test

Q. ID: ITISKILL9172VI

March 2026

Govt ITI Yadahalli

Answer Key

Duration: 20 Mins

Total Marks: 10

Q.ID: ITISKILL9172VI

1. What is the difference of Colpitts oscillator compare to Hartley oscillator?

- A) Uses crystal oscillator
- B) Uses split capacitor
- C) Uses SCR combination
- D) Uses split inductor

**Answer: B) Uses split capacitor**

2. Which is the 3 terminal, negative voltage regulator IC?

- A) IC 7812
- B) IC 7905
- C) LM 340
- D) LM 320

**Answer: B) IC 7905**

3. Which is the transistor used to operate the Colpitts oscillator?

- A) BC 148B
- B) BF 194B
- C) AC 188
- D) AC 127

**Answer: B) BF 194B**

4. Which circuit is determined by the frequency of LC tank circuit?

- A) Amplifier
- B) Oscillator
- C) Demodulator
- D) Multiplexed

**Answer: B) Oscillator**

5. How to improve the frequency stability in oscillator circuits?

- A) Using L and C
- B) By using quartz crystal
- C) Improve the property of circuits
- D) Increase the supply voltage

**Answer: B) By using quartz crystal**

6. How many transistors are built inside the Very Large Scale

Integration (VLSI) IC package?

- A) 1000 and above
- B) 1 to 10 transistors
- C) 100 to 1000 transistors
- D) 10 to 100 transistors

**Answer: A) 1000 and above**

7. Which circuits commonly use parallel-fed Hartley oscillators?

- A) Automatic voltage stabilizers
- B) Radio receivers
- C) Stereo amplifiers
- D) Television receivers

**Answer: B) Radio receivers**

8. How many time constant period is required to fully charge a capacitor?

- A) 10 time constants
- B) 7 time constants
- C) 5 time constants
- D) 3 time constants

**Answer: C) 5 time constants**

9. Why LC tuned circuits are not used in audio frequency oscillators?

- A) LC tank circuit does not produce AF signals
- B) LC components are not available
- C) LC tank circuit operation requires high voltage
- D) LC values required is too large

**Answer: D) LC values required is too large**

10. How much is the maximum load current of the negative voltage regulator IC 7912?

- A) 0.55 A
- B) 1.5 A
- C) 1.0 A
- D) 2.0 A

**Answer: D) 2.0 A**