

**Duration: 30 Mins**

**Total Marks: 25**

**Q.ID: ITISKILL9897HH**

1. What is the overall base emitter voltage required to turn the darlington pair?

- A) 1.4 V
- B) 0.7 V
- C) 0.2 V
- D) 0.3 V

**Answer: A) 1.4 V**

2. What is the voltage gain in a transistor if the input voltage in 40mv and the output voltage in 3.6V?

- A) 270
- B) 90
- C) 45
- D) 180

**Answer: B) 90**

3. What in the current gain of a common ? base amplifier?

- A) Greater than 1
- B) Less than 1
- C) Unity
- D) Infinity

**Answer: B) Less than 1**

4. Which parameter of passive component can be calculated using the formula ?

- A) Capacitance
- B) Inductance
- C) Inductive reactance
- D) Capacitive reactance

**Answer: D) Capacitive reactance**

5. What is the name of multi-stage amplifiers?

- A) Complementary symmetry amplifier
- B) Cascaded amplifier
- C) Cascoded amplifier
- D) Darlington pair amplifier

**Answer: B) Cascaded amplifier**

6. What type of packaging is generally used to transistors utilized for low power amplification?

- A) Plastic packaging with metal heatsinks
- B) Metal packaging
- C) Ceramic packaging
- D) Plastic packaging

**Answer: D) Plastic packaging**

7. Which type of amplifier is used to operate the loud speaker?

- A) Power amplifier
- B) IF amplifier
- C) RF amplifier
- D) Voltage amplifier

**Answer: A) Power amplifier**

8. Which configuration of transistor amplifier is most commonly used in electronic circuits?

- A) Common collector configuration
- B) Common emitter configuration
- C) Common base configuration
- D) Common drain amplifier configuration

**Answer: B) Common emitter configuration**

9. What is the formula used to calculate the current gain (alpha) of common base amplifier?

- A)  $I_C / I_E$
- B)  $I_B / I_E$
- C)  $I_E / I_C$
- D)  $I_E / I_C$

**Answer: A)  $I_C / I_E$**

10. What is the advantage of using bias in transistor circuits?

- A) Provides positive feedback
- B) Gives maximum distortion
- C) Easily sets saturated
- D) Never reach saturation

**Answer: D) Never reach saturation**

11. How does the values of bias resistors selected for collector current in class -B amplifiers?

- A) Quiescent current beyond the cut-off point
- B) Quiescent current over the cut-off value
- C) Quiescent current at mid point
- D) Q point set slightly below cut-off

**Answer: B) Quiescent current over the cut-off value**

12. Why NPN type of transistors are preferred over the PNP type transistors?

- A) NPN has higher switching speed
- B) NPN has lower switching speed
- C) Low operating voltage
- D) NPN has good bias stability

**Answer: A) NPN has higher switching speed**

13. What is the meaning of first letter indicated in the transistor code number BC 107?

- A) Indium material used
- B) Silicon material used
- C) Antimony material used
- D) Germanium material used

**Answer: B) Silicon material used**

14. How the maximum permissible voltage that can be applied across the collector ? Emitter junction of a transistor is indicated?

- A) VCB (max) in volts
- B) VCC in volts
- C) VCE (max) in volts
- D) VBE (max) in volts

**Answer: C) VCE (max) in volts**

15. Which type of packaging is used to transistors utilized for medium power amplification?

- A) Metal packaging
- B) Plastic packaging
- C) Plastic packaging with metal heatsinks
- D) Ceramic packaging

**Answer: C) Plastic packaging with metal heatsinks**

16. What is the maximum emitter to base voltage VEB (max) for the transistor BC 147?

- A) 8V
- B) 5V
- C) 4V
- D) 6V

**Answer: D) 6V**

17. Where does the depletion region exist in a bipolar transistor?

- A) Between collector and emitter electrodes
- B) Between collector - base electrodes
- C) Between emitter - base electrodes
- D) Between E-B and B-C electrodes

**Answer: D) Between E-B and B-C electrodes**

18. Which class of amplifier uses fixed bias because of its important advantage of transistor will never go to saturation?

- A) Class - C
- B) Class - A
- C) Class - AB
- D) Class - B

**Answer: B) Class - A**

19. Which type of transistors are required to amplify signals from the microphone /transducer?

- A) Epitaxial versawatt transistors
- B) Medium power transistors
- C) Low power transistors
- D) High power transistors

**Answer: C) Low power transistors**

20. In which quantity affects the Q point of a transistor

amplifier?

- A) Mismatching signals
- B) Increased temperature
- C) Proper biasing methods
- D) Decreased temperature

**Answer: B) Increased temperature**

21. What is the current gain of common collector amplifier?

- A) Medium
- B) Very high
- C) High
- D) Low

**Answer: B) Very high**

22. What will happen when the forward bias voltage across the PN junction is increased excessively?

- A) Barrier width of junction increases
- B) No current flows through the junction
- C) Increases the cut-in voltage
- D) Junction ruptured and short circuited

**Answer: D) Junction ruptured and short circuited**

23. What is the input impedance of darlington pair transistors?

- A) Uniter
- B) Very low input impedance
- C) Very high input impedance
- D) Medium input impedance

**Answer: C) Very high input impedance**

24. Why transistors made of silicon is preferred over the germanium semiconductor material?

- A) Silicon transistor needs low cut-in-voltage
- B) Requires complicated bias arrangement
- C) Higher thermal stability
- D) Complex design

**Answer: C) Higher thermal stability**

25. How can you confirm a transistor as defective?

- A) By physical testing
- B) By ohm meter testing
- C) By voltage measurements
- D) By circuit testing

**Answer: B) By ohm meter testing**