

# Monthly test for month of February-2026

Q. ID: ITISKILL9966RT

Trade theory

February 2026

Varma ITI KOLLEGAL

Question Paper

Student: **SANJAY S Electric machanic**

Score: **16/25 (64.00%)**

Code: **8618**

1. How many transistors are built inside the Very Large Scale Integration (VLSI) IC package?  
A) **1000 and above** B) 1 to 10 transistors  
C) 10 to 100 transistors D) 100 to 1000 transistors (Incorrect)
2. Which IC package consist of 100 to 1000 transistors?  
A) **Large scale integration (LSI)** B) Small scale integration (SSI)  
C) Medium scale integration (MSI) (Incorrect) D) Very large scale integration (VLSI)
3. Which is the 3 terminal, negative voltage regulator IC?  
A) LM 320 B) LM 340  
C) **IC 7905** D) IC 7812 (Incorrect)
4. Which three terminal voltage regulator IC has adjustable output?  
A) LM 100 B) LM 105  
C) LM 305 D) **LM 317 (Correct)**
5. How much is the maximum load current of the negative voltage regulator IC 7912?  
A) 1.0 A B) 1.5 A  
C) **2.0 A (Correct)** D) 0.55 A
6. What is the current rating of voltage regulator IC LM338K?  
A) 2A B) 3A  
C) 4A D) **5A (Correct)**
7. Which method is followed to troubleshoot the problem causing section by the symptom?  
A) Step by step method B) Sensory test method  
C) Trial and error method D) **Logical approach method (Correct)**
8. What is the current rating of voltage regulator IC LM317L?  
A) **0.1 A** B) 0.2 A (Incorrect)  
C) 0.3 A D) 0.4 A
9. What is the range of output voltage of regulator IC LM 317?  
A) 0 to 25 V B) 0 to 30 V  
C) 0 to 32 V D) **1.2 V to 32 V (Correct)**
10. Which type of voltage regulator is IC 723?  
A) Multipin variable voltage regulator (Incorrect) B) Three pin positive voltage regulator  
C) Three pin negative voltage regulator D) **Three pin adjustable voltage regulator**
11. What is the natural shape of a quartz crystal?  
A) Cylindrical shape with pyramid at ends B) Cube shape with pyramid at ends  
C) Pentagonal prism with pyramid at ends D) **Hexagonal prism with pyramid at ends (Correct)**
12. What is the difference of Colpitts oscillator compare to Hartley oscillator?  
A) Uses split inductor B) **Uses split capacitor**  
C) Uses crystal oscillator (Incorrect) D) Uses SCR combination
13. What is the percentage of charge accumulated by the capacitor at the end of 2 time constant limit?  
A) 0.4 B) 0.5  
C) 0.632 D) **0.864 (Correct)**
14. How many time constants required to change a capacitor to 63.2% of its full charge voltage?  
A) Four time constant B) Three time constant  
C) Two time constant D) **One time constant (Correct)**
15. What type of arrangement is required to sustain the oscillations of the oscillator circuit?  
A) Provide negative feedback B) **Provide regenerative feedback (Correct)**  
C) Increase the bias voltage D) Increase the value of inductor
16. What type of feed back is used by the Wein-bridge oscillator to oscillate the signal?  
A) No feedback B) Positive feedback

C) Negative feedback

**D) Both positive and negative feedback (Correct)**

C) LC tank circuit does not produce AF signals

D) LC tank circuit operation requires high voltage

17. How to improve the frequency stability in oscillator circuits?

- A) Increase the supply voltage
- C) Using L and C

**B) By using quartz crystal (Correct)**  
D) Improve the property of circuits

21. How many degrees is equal to one radian?

- A)  $(\pi)/(360)$
- C)  $(\pi)/(180)$

B)  $(360)/(\pi)$   
**D)  $(180)/(\pi)$  (Correct)**

18. Which is the transistor used to operate the Colpitts oscillator?

- A) AC 127
- C) BC 148B

**B) BF 194B (Correct)**  
D) AC 188

22. Which is equal to  $\sin \theta$ ?

- A) Opposite Side/Hypotenuse (Correct)**
- C) Adjacent Side/Hypotenuse

B) Hypotenuse/Opposite side  
D) Hypotenuse/Adjacent side

19. How to overcome the problem of frequency drift in LC oscillators?

- A) Apply opposite polarity of signal
- B) Provide negative feedback signal
- C) Using high Q coils and good quality capacitors (Correct)**
- D) Increase the supply voltage

23. What is equal to  $\cos \theta$ ?

- A) Hypotenuse/Adjacent Side (Incorrect)
- C) Opposite side/Hypotenuse

**B) Adjacent Side/Hypotenuse**  
D) Hypotenuse/Opposite Side

20. Why LC tuned circuits are not used in audio frequency oscillators?

- A) LC values required is too large (Correct)**
- B) LC components are not available

24. What is equal to  $\tan \theta$ ?

- A) Opposite Side/Hypotenuse
- C) Opposite Side/Adjacent Side**

B) Adjacent Side/Hypotenuse (Incorrect)  
D) Adjacent side/Opposite side

25. What is the value of  $\tan \theta$  if  $\sin \theta = 4/5$  ?

- A)  $(4/5)$
- C)  $(3/4)$  (Incorrect)

B)  $(5/3)$   
**D)  $(4/3)$**