

Duration: 30 Mins

Total Marks: 6

Q.ID: ITISKILL2774ZX

1. What is the name of the gate | ಗೇಟ್ ಹೆಸರೇನು?



- A) AND Gate | AND ಗೇಟ್      B) OR Gate | OR ಗೇಟ್  
C) NOT Gate | NOT ಗೇಟ್      D) Ex-NOR Gate | Ex-NOR ಗೇಟ್


Answer: A) AND Gate | AND ಗೇಟ್

2. What is the fuse rate to run a 10 HP in three phase induction motor at full load? | ಫುಲ್ ಲೋಡ್‌ನಲ್ಲಿ ಮೂರು ಫೇಸ್ ಇಂಡಕ್ಷನ್ ಮೋಟಾರ್‌ನಲ್ಲಿ 10 HP ಅನ್ನು ಚಲಾಯಿಸಲು ಫ್ಯೂಸ್ ರೇಟ್ ಎಷ್ಟು?

- A) 10 A      B) 30 A  
C) 15 A      D) 25 A

Answer: D) 25 A

3. Identify the symbol used for microphone (general) in electrical and electronic circuits. | ಎಲೆಕ್ಟ್ರಿಕಲ್ ಮತ್ತು ಎಲೆಕ್ಟ್ರಾನಿಕ್ ಸರ್ಕ್ಯೂಟ್‌ಗಳಲ್ಲಿ ಮೈಕ್ರೋಫೋನ್ (ಸಾಮಾನ್ಯ) ಗಾಗಿ ಬಳಸುವ ಚಿಹ್ನೆಯನ್ನು ಗುರುತಿಸಿ.

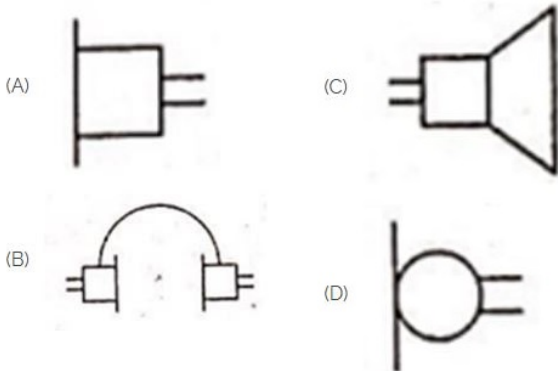

- A) B      B) A  
C) D      D) C

Answer: C) D

4. To apply for a job, what is the next step after making an impactful resume?

- A) Writing an impressive cover letter      B) Preparing for interview  
C) Applying for the job      D) Sending the resume to the employer


Answer: A) Writing an impressive cover letter

5. Which of the following are included in a resume?

- A) Childhood memories, dreams, and aspirations      B) Hobbies, favorite foods, and personal interests  
C) Contact information, educational details, skills and work experience      D) Daily routine, favorite movies, and vacation plans

Answer: C) Contact information, educational details, skills and work experience

6. Which is a symbol of DC motor? | DC ಮೋಟಾರ್‌ನ ಸಂಕೇತ ಯಾವುದು?

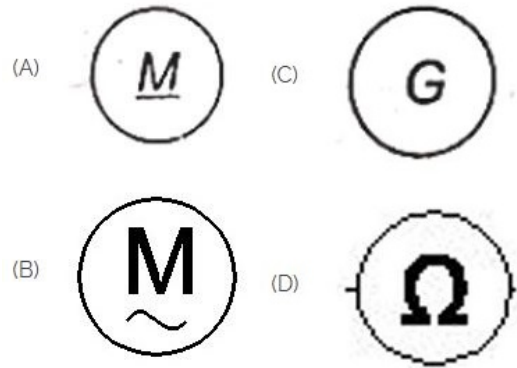

- A) C      B) B  
C) D      D) A

Answer: D) A